


Конечные автоматы Диаграммы состояний Рекомендации по стилю кодирования

Дмитрий Смехов

Концепция конечного автомата на ПЛИС

Представление алгоритмов в виде конечных автоматов

Александр Силаньев <https://youtu.be/MDkaXKM5XYI>

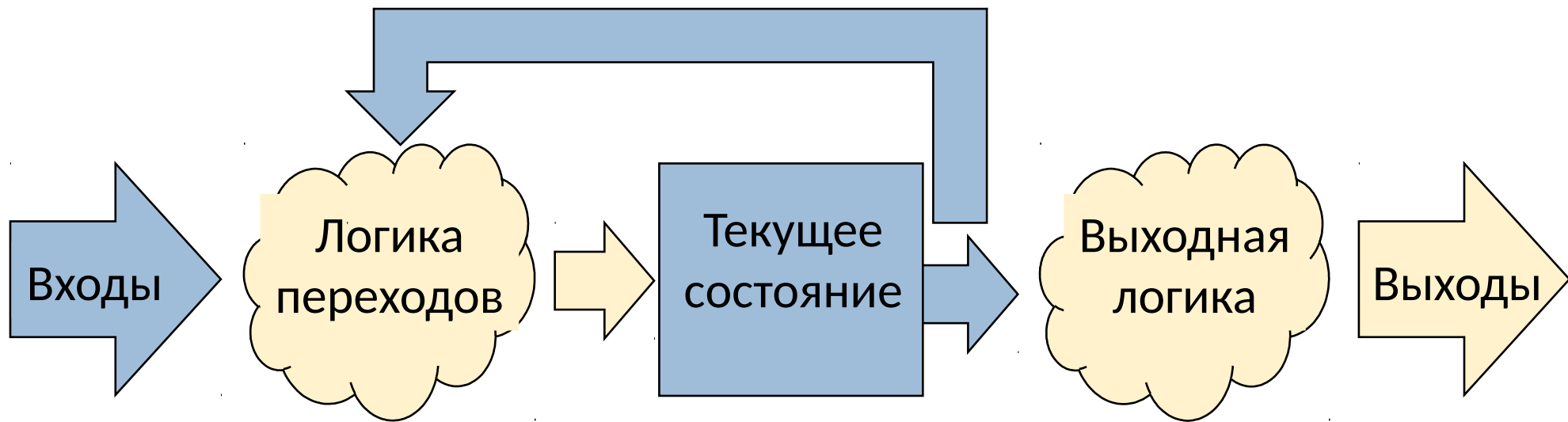



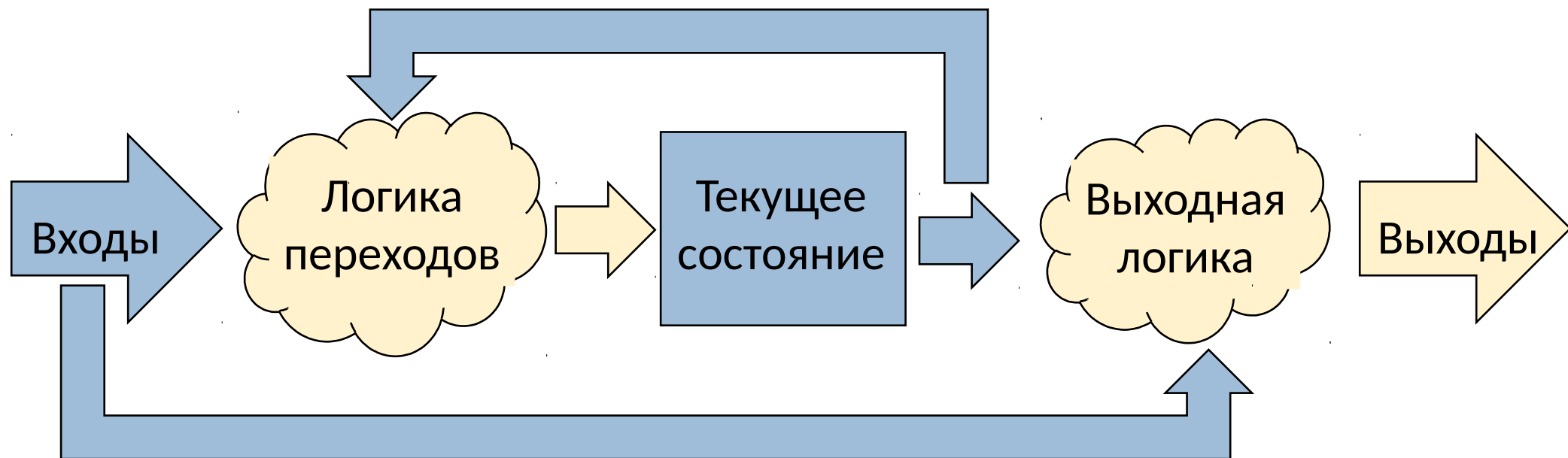


Диаграмма состояния автомата Мура

 

S_1 и S_2 — состояния. Дуги помечены входными сигналами

Диаграмма состояния автомата Мили

 

S_0, S_1, S_2 — состояния.
Дуги помечены как j / k
 j — входные данные
 k — выходные данные

Реализация на SystemVerilog

```
logic [0:0]  state;
```

```
always_ff @(posedge clk) begin
    if( rstp ) begin
        state <= # 1 0;
        c <= #1 0;
    end else begin
        case( state )
            0: begin
                c <= #1 0;
                if( a )
                    state <= #1 1;
            end
            1: begin
                c <= #1 1;
                if( ~a )
                    state <= #1 0;
            end
        endcase
    end
end
```

```
logic [0:0]  state;
```

```
always_ff @(posedge clk) begin
    case( state )
        0: begin
            c <= #1 0;
            if( a )
                state <= #1 1;
        end
        1: begin
            c <= #1 1;
            if( ~a )
                state <= #1 0;
        end
    endcase

    if( rstp )
        state <= # 1 0;
end
```

Два always блока

```
logic [0:0]  state;  
logic [0:0]  next_state;
```

```
always_ff @(posedge clk) begin  
    if( rstp )  
        state <= # 1 0;  
    else  
        state <= # 1 next_state;  
end
```

```
always_comb begin  
    case( state )  
    0: begin  
        c = 0;  
        if( a ) begin  
            next_state = 1;  
        end  
  
    1: begin  
        c = 1;  
        if( ~a ) begin  
            next_state = 0;  
        end  
  
    end  
  
end
```

Это автомат Мура. Выходы не регистровые

Два always блока — автомат Мили

```
logic [0:0]  state;  
logic [0:0]  next_state;
```

```
always_ff @(posedge clk) begin  
    if( rstp )  
        state <= # 1 0;  
    else  
        state <= # 1 next_state;  
end
```

```
always_comb begin  
    case( state )  
    0: begin  
        c = 0;  
        if( a ) begin  
            c=1;  
            next_state = 1;  
        end  
    end  
    1: begin  
        c = 1;  
        if( ~a ) begin  
            next_state = 0;  
        end  
    end  
end
```

Это автомат Мили. Выходы не регистровые

В данном примере во время действия rstp выходной сигнал c может быть равен 1

Два always блока — сложная логика

```
logic [0:0]  state;  
logic [0:0]  n_state;
```

```
always_ff @(posedge clk) begin
```

```
    if( rstp ) begin  
        cnt <= #1 0;  
        state <= # 1 0;  
    end else begin  
        cnt <= #1 n_cnt;  
        state <= # 1 n_state;  
    end
```

```
end
```

```
always_comb begin
```

```
    n_state = state;  
    n_cnt = cnt;
```

```
    if( a )  
        n_state = 1;
```

```
    if( 1==n_state ) begin  
        n_cnt++;  
    end
```

```
    if( b )  
        n_cnt=0;
```

```
    if( 10==n_cnt )  
        n_state = 0;
```

```
end
```