


Простые последовательностые схемы

Дмитрий Смехов

HDL, RTL and FPGA: Part 2

<https://bit.ly/2022-08-02-verilog-2-bishkek-yuri-panchul>

D-триггер

 


Логическое И


D	S	R	C	Q	QB
X	X	1	X	0	1
X	1	0	X	1	0
0	0	0	R	0	1
1	0	0	R	1	0

Фронт сигнала.
Переход из 0 в 1.


D-триггер — фиксация данных

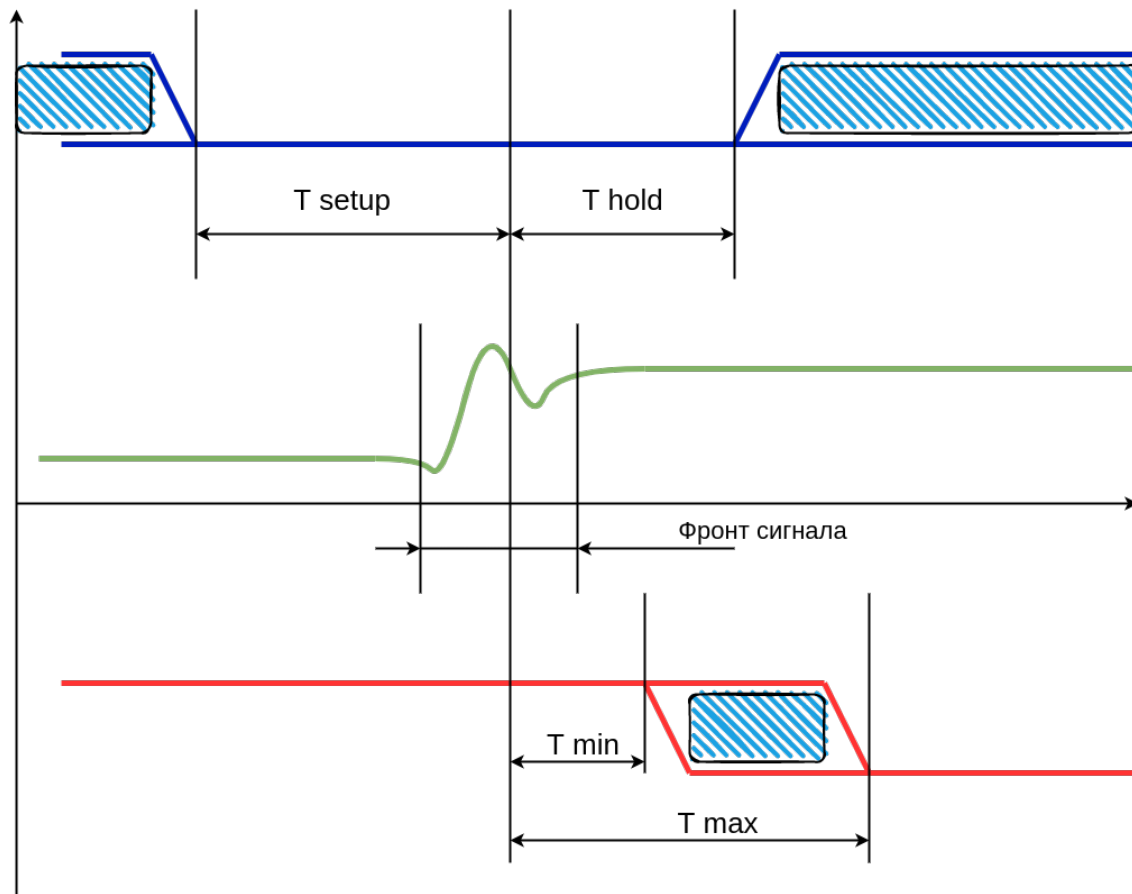


Синхронные схемы

 


Временная диаграмма

 

Метастабильность

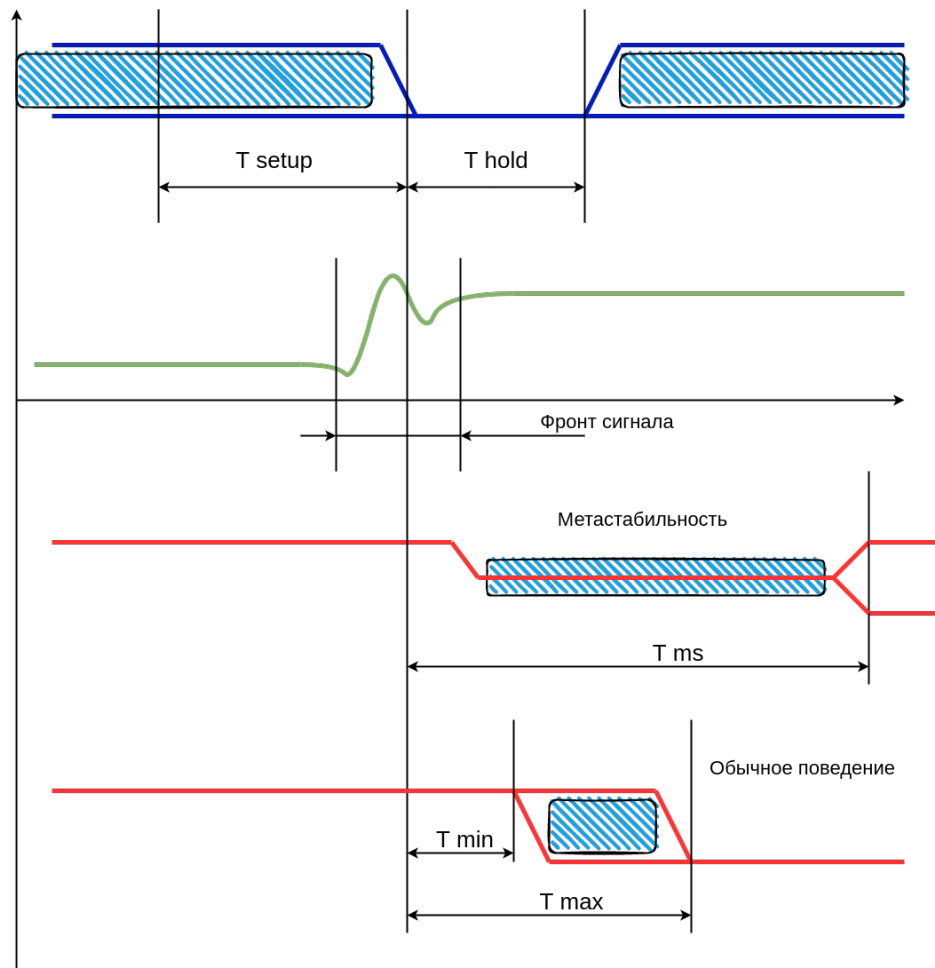

 

- Регистр
- Сдвиговый регистр
- Счётчик
- Конечный автомат
- FIFO
- Кредитный счётчик

Параллельный регистр

```

module(
    input wire          clk,
    input wire          rstp,
    input wire          enable,
    input  wire [31:0]  data,
    output wire [31:0]  reg_data_o
);
logic [31:0]          reg_data;


always_ff @(posedge clk) begin

    if( rstp )
        reg_data <= #1 32'h0;
    else if( enable )
        reg_data <= #1 data;
end

assign reg_data_o = reg_data;

endmodule

```

 


```
module(  
    input wire          clk,  
    input wire          rstp,  
    input wire          cnt_en,  
    output wire [31:0]  cnt_o  
);  
  
    logic [31:0]        cnt;  
  
    always_ff @(posedge clk) begin  
  
        if( rstp )  
            cnt <= #1 32'h0;  
        else if( cnt_en )  
            cnt <= #1 cnt+1;  
    end  
  
    assign cnt_o = cnt;  
  
endmodule
```

Реализация счётчика

Сумматор

CI	A	B	CO	Q
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


Adder + Register = Counter


- A group of D-flip-flops is called a register.
- Do not confuse with Verilog `reg` or CPU registers in programming.
- In this code the result of addition is stored to use in the next clock cycle.


```
module counter
(
    input                clock,
    input                reset_n,
    output reg [31:0] count
);

 always @(posedge clock or negedge reset_n)
begin
    if (!reset_n)
        count <= 32'b0;
    else
        count <= count + 32'b1;
end
```




 The register contains 0, it gets propagated to the adder.




 

 
0 enters the adder. The adder's output is not stable yet.



 
The adder computed $0 + 1 = 1$. Register still contains 0.



 
Positive edge of the clock is coming. Register is still 0.



 
The aperture time. Register is about to store 1.



 
The register recorded 1 and is about to propagate it outside.



 
The current state is 1, it gets propagated to the adder.



 
1 enters the adder. The adder's output is not stable yet.



 
The adder computed $1 + 1 = 2$. The register still contains 1.



 
A positive edge of the clock is coming. The register is still 1.



 
The aperture time. The register is about to store 2.



 The register recorded 2 and is about to propagate it outside.



 The current state is 2, it gets propagated to the adder.



Сдвиговый регистр

```

module(
    input wire          clk,
    input wire          rstp,
    input wire          shift_en,
    output wire [3:0]   reg_data_o
);
    logic [3:0]         reg_data;

    always_ff @(posedge clk) begin
        if( rstp )
            reg_data <= #1 4'b0001;
        else if( shift_en ) begin
            reg_data[0] <= #1 reg_data[3];
            reg_data[3:1] <= #1 reg_data[2:0];
        end
    end

    assign reg_data_o = reg_data;
endmodule

```

